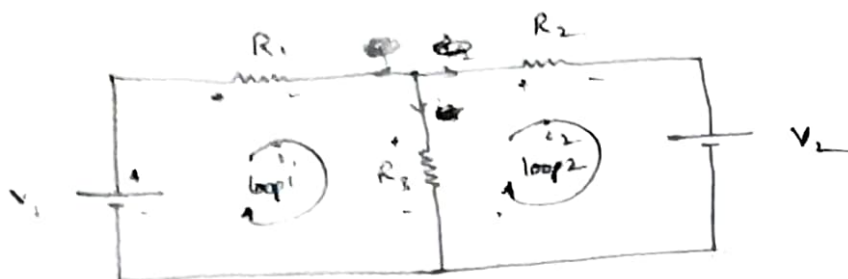



★

Mesh Analysis



- Assume CW or ACW dirⁿ in loops
- form equations in i_1, i_2 , etc. by KVL in individual loops
- Solve & find i_1, i_2 , etc...

Loop ①

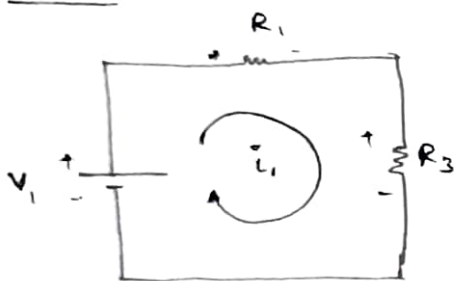


$$-i_1 R_1 - (i_1 - i_2) R_3 + V_1 = 0$$

$$V_1 = i_1 R_1 + (i_1 - i_2) R_3$$

$$V_1 = i_1 R_1 + i_1 R_3 - i_2 R_3$$

$$V_1 = i_1 (R_1 + R_3) - i_2 R_3 \quad \text{--- (1)}$$

Loop ②

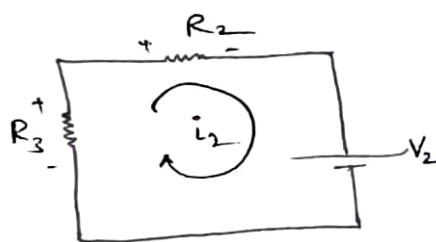


$$+ (i_2 - i_1) R_3 - i_2 R_2 - V_2 = 0$$

$$V_2 = i_2 R_3 - i_2 R_2 - i_1 R_3$$

$$V_2 = i_2 (R_3 - R_2) - i_1 R_3 \quad \text{--- (2)}$$

Solve both & find answers (required one's).

Problem

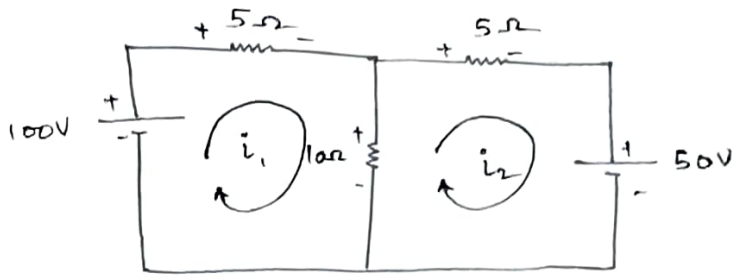

Ans

Loop ①

$$100 - 5i_1 - 10(i_1 - i_2) = 0$$

$$100 - 5i_1 - 10i_1 + 10i_2 = 0$$

$$-15i_1 + 10i_2 = -100$$

$$15i_1 - 10i_2 = 100$$

$$3i_1 - 2i_2 = 20$$

$$6i_1 - 4i_2 = 40$$

$$+6i_1 - 9i_2 = 30$$

$$-5i_2 = -10$$

$$i_2 = 2A$$

$$i_2 = 2A$$

Loop ②

$$-5i_2 - 50 + 10(i_2 - i_1) = 0$$

$$-5i_2 - 50 + 10i_2 - 10i_1 = 0$$

$$-15i_2 + 10i_1 = 50$$

$$-3i_2 + 2i_1 = 10$$

$$3i_1 - 4i_2 = 20$$


$$3i_1 = 24$$

$$i_1 = 8A$$



$$i_3 = i_1 - i_2 = 6A$$

* Source Transformations

1) Voltage source to current source

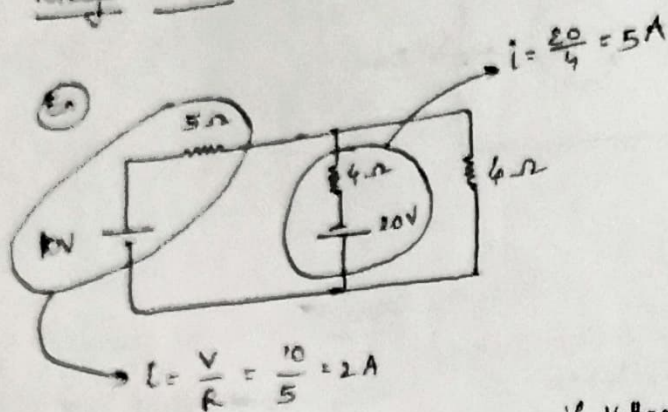


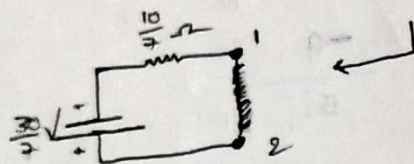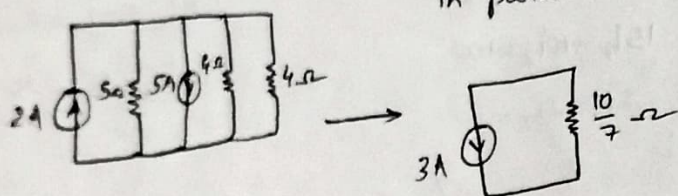if Voltage & resistor in series
replace with current & resistance
in parallel.



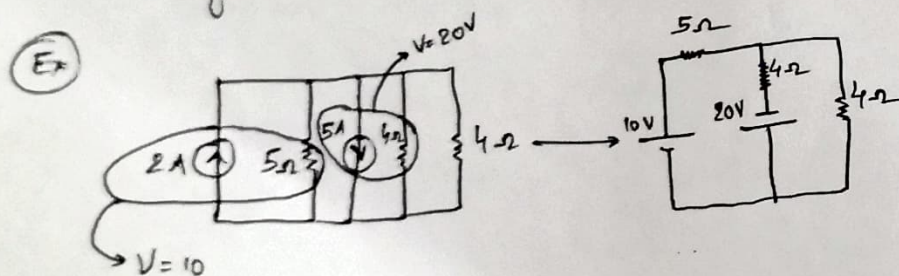2) Current source to voltage source

If current & resistor are in parallel then replace it with
voltage & resistor in series



* Super-position Theorem

→ It is just like love pinki gets from her n no. of boyfriends.

$$\text{Total love} = L_1 + L_2 + L_3 + \dots$$


→ And also love of Boyfriend 1 does not depend on love of other boyfriends.

→ Each love to pinki is independent from all other loves pinki gets.

Definition

→ The voltage/current across an element in a linear circuit is algebraic sum of voltages/current across that element due to each independent source acting alone.

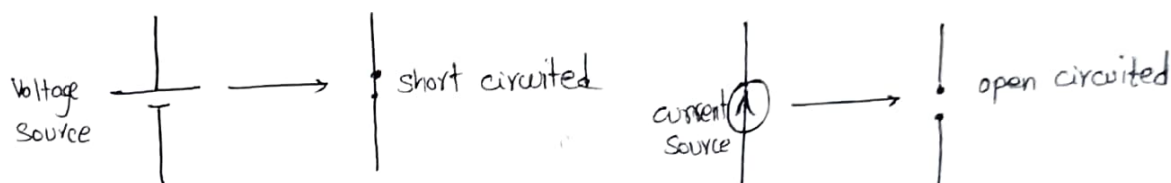
→ Each independent source is either open circuited / short circuited.



→ Do not turn off dependent sources

→ Theorem is not valid for non-linear circuits.

Example Problem

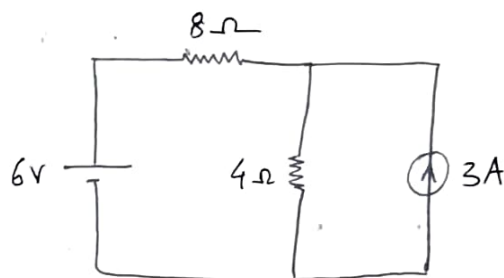



Find voltage across 4Ω resistor

Ans

$$V_{4\Omega} = (V_{4\Omega})_{PD} + (V_{4\Omega})_I$$

Case ①

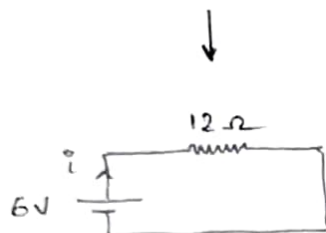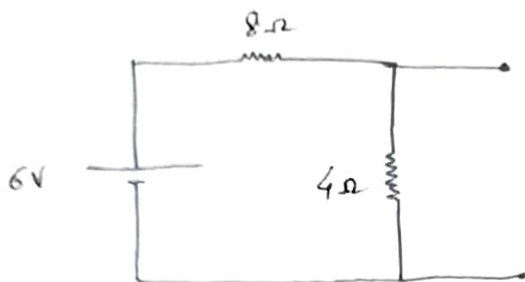For $(V_{4\Omega})_{PD} \rightarrow$ remove current source \rightarrow Open circuit




$$i = \frac{V}{R} = \frac{6}{12} = 0.5 \text{ A}$$

$$(V_{4\Omega})_{PD} = i_{4\Omega} \times 4 = 0.5 \times 4 = 2 \text{ V}$$

$$(V_{4\Omega})_{PD} = 2 \text{ V}$$

Case ②

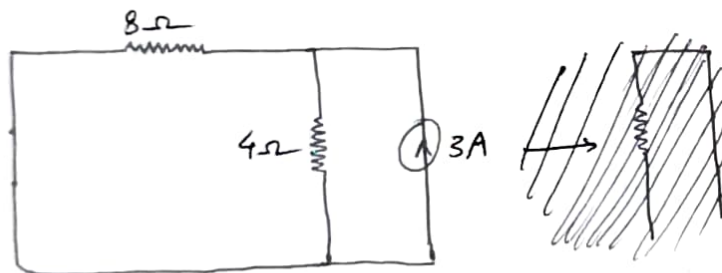For $(V_{4\Omega})_I \rightarrow$ remove voltage source \rightarrow Short Circuit



Applying Current division rule

$$i_{4\Omega} = 3 \times \frac{8}{8+4} = 3 \times \frac{8}{12} = 2 \text{ A}$$

$$(V_{4\Omega})_I = 8 \text{ V}$$

$$i_{4\Omega} = 2 \text{ A} \rightarrow (V_{4\Omega})_I = i_{4\Omega} \times 4 = 2 \times 4 = 8$$

Answer


$$V_{4\Omega} = 2 + 8 = 10 \rightarrow V_{4\Omega} = 10 \text{ V}$$

* Norton's Theorem

- A linear & bidirectional 2 terminal network can be replaced by an equivalent circuit consisting of current source I_N in parallel with resistor R_N .
- To find I_N → short circuit current through terminals
- To find R_N → Input resistance at terminals when independent sources are turned off
- Finally replace circuit with Eq. circuit with load resistance in parallel.

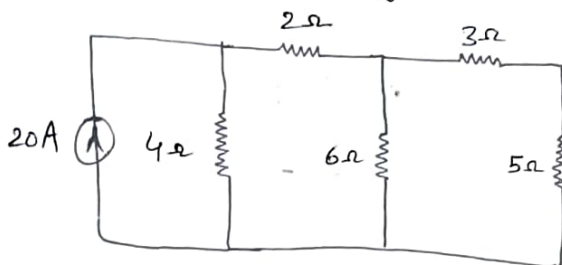
Example Problem

Find current flowing through 5Ω Resistance.



Ans


To find I_N

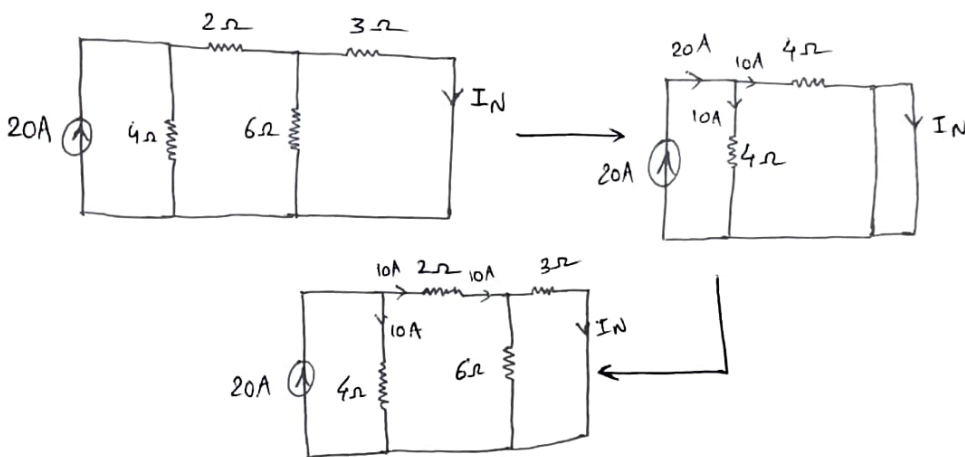

$$I_N = 10 \times \frac{6}{6+3} = 10 \times \frac{6}{9} = \frac{20}{3} \text{ A}$$


$$I_N = \frac{20}{3} \text{ A}$$

To find R_N

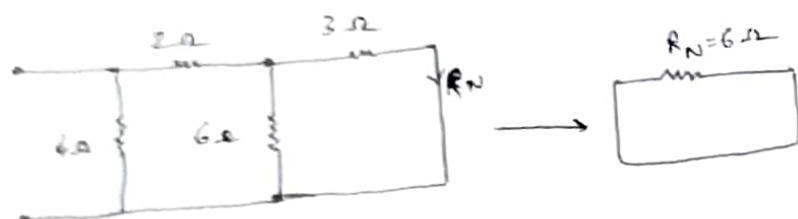

$$R_N = 6\Omega$$

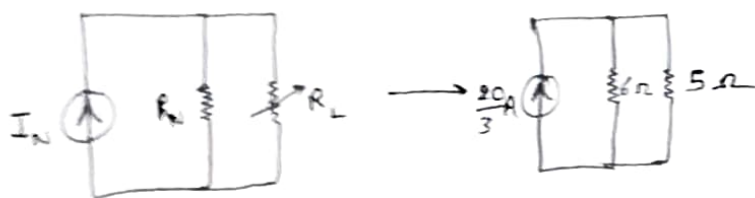Now replace given circuit with eq circuit then attach load resistance in parallel



$$i_{5\Omega} = \frac{20}{3} \times \frac{6}{6+5} = \frac{40}{11} \text{ A}$$


$$i_{5\Omega} = \frac{40}{11} \text{ A}$$

→ Hence by Norton's Theorem.

* Thevenin Theorem

- A linear bidirectional 2 terminal n/w can be replaced by an equivalent circuit consisting V_{th} & R_{th} with a load resistance in series.
- To find V_{th} → open circuit voltage at terminals
- To find R_{th} → Input resistance at terminals when all independent sources are off.
- Finally replace with eq. circuit with R_L in series


Example Problem

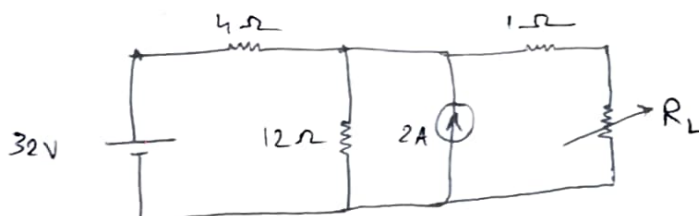

Find current flowing through load resistance when it is (i) 6Ω
(ii) 16Ω

Ans

To find V_{th}

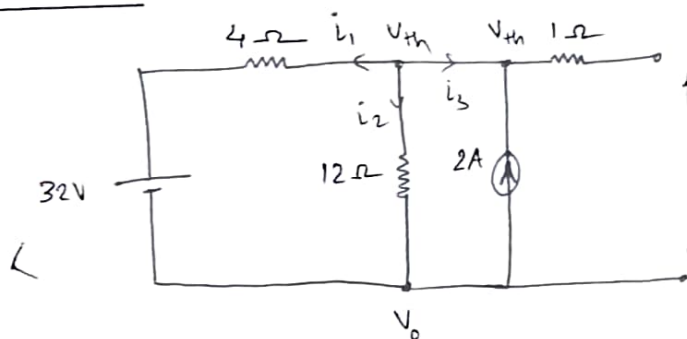

V_{th} should be here but due to open circuit it is placed as shown.

Applying KCL

$$\frac{V_{th} - 32}{4} + \frac{V_{th} - 0}{12} + (-2) = 0$$


$$3V_{th} - 96 + V_{th} - 24 = 0 \Rightarrow 4V_{th} = 120 \Rightarrow \boxed{V_{th} = 30V}$$

To find R_a




$$R_{th} = 4 \Omega$$

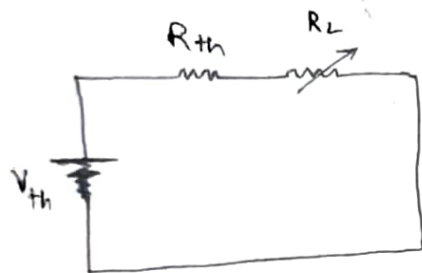
Now replace given circuit with eq circuit consisting of V_{th} , R_{th} and load resistance in series.



(i) $R_L = 6 \Omega$

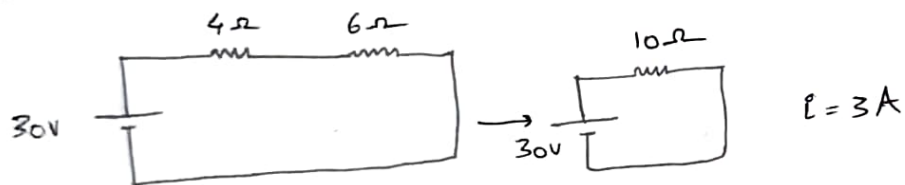


(ii) $R_L = 16 \Omega$

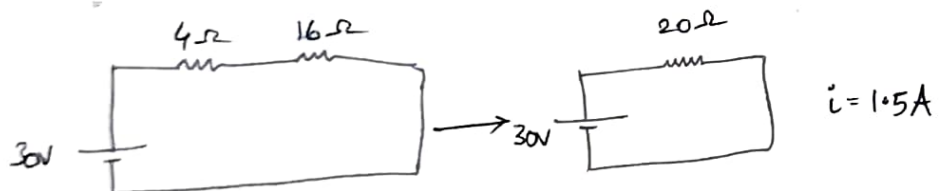

(*) Star to Delta Connection
 (λ) (Δ)

(Ex)

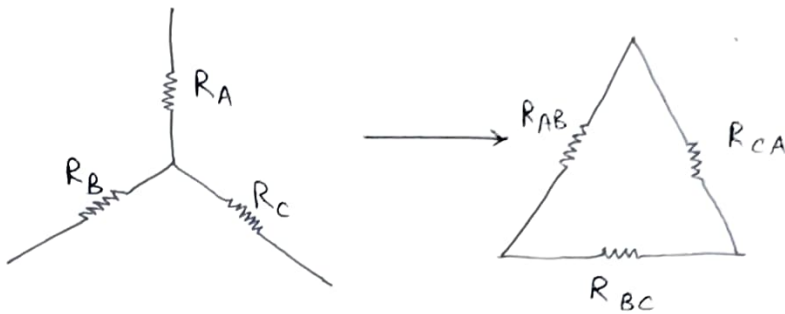


$$R_{AB} = \frac{R_A R_B + R_B R_C + R_C R_A}{R_C}$$

$$R_{BC} = \frac{R_A R_B + R_B R_C + R_C R_A}{R_A}$$

$$R_{CA} = \frac{R_A R_B + R_B R_C + R_C R_A}{R_B}$$

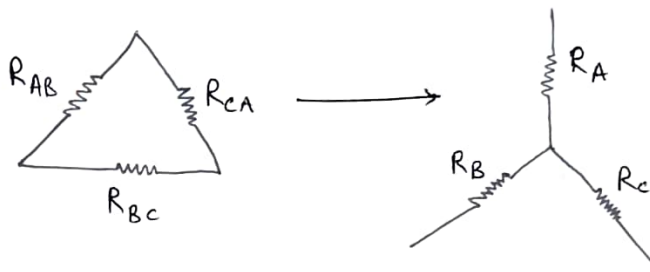(*) Delta to Star Connection
 (Ex) (Δ) (λ)




$$R_A = \frac{R_{AB} \times R_{CA}}{R_{AB} + R_{BC} + R_{CA}}$$

$$R_B = \frac{R_{AB} \times R_{BC}}{R_{AB} + R_{BC} + R_{CA}}$$


$$R_C = \frac{R_{BC} \times R_{CA}}{R_{AB} + R_{BC} + R_{CA}}$$

Problem


Method ① Find current through circuit

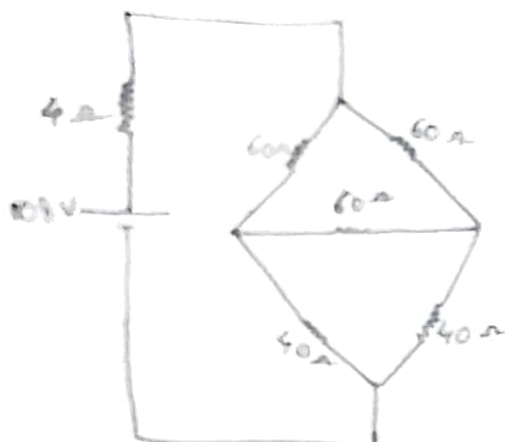

Let us convert Δ of 60Ω into λ

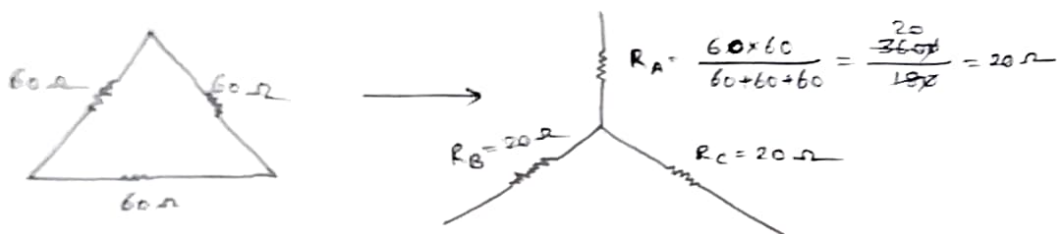


So finally

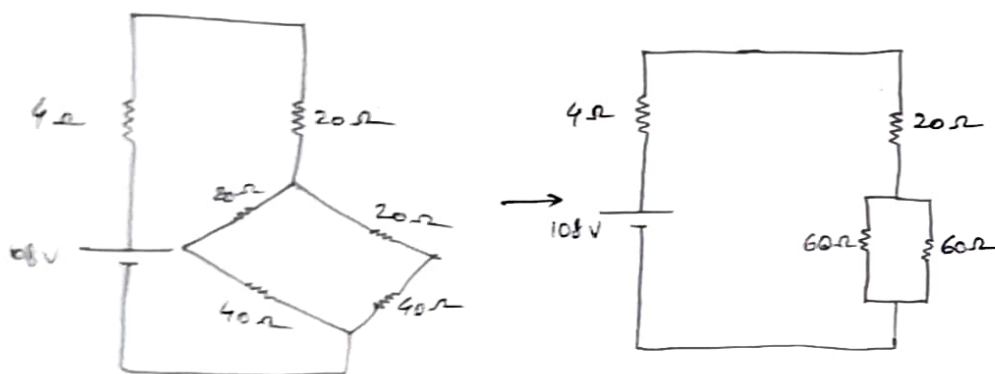


$$I = \frac{V}{R} = \frac{108}{54} = 2A$$


$$I = 2A$$

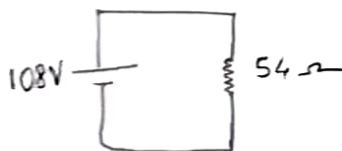



Method ②

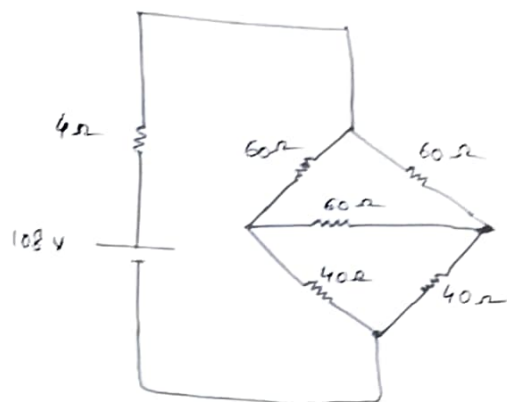

Let us convert Δ to λ

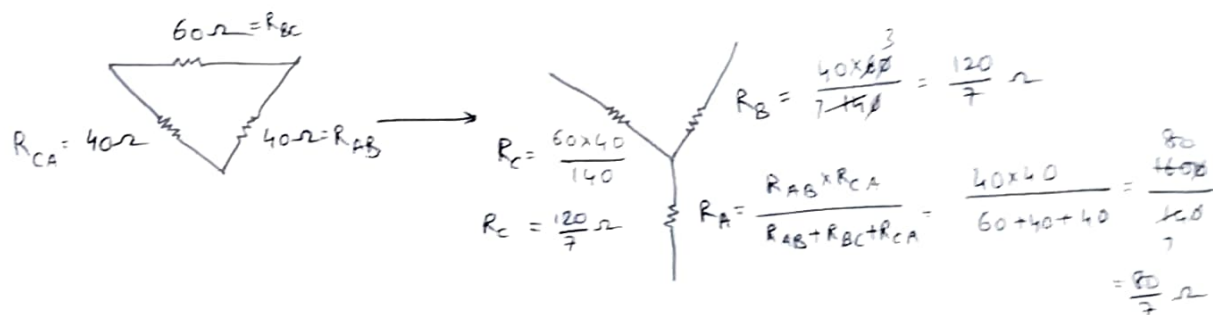


So Finally

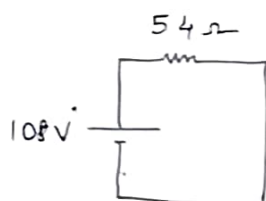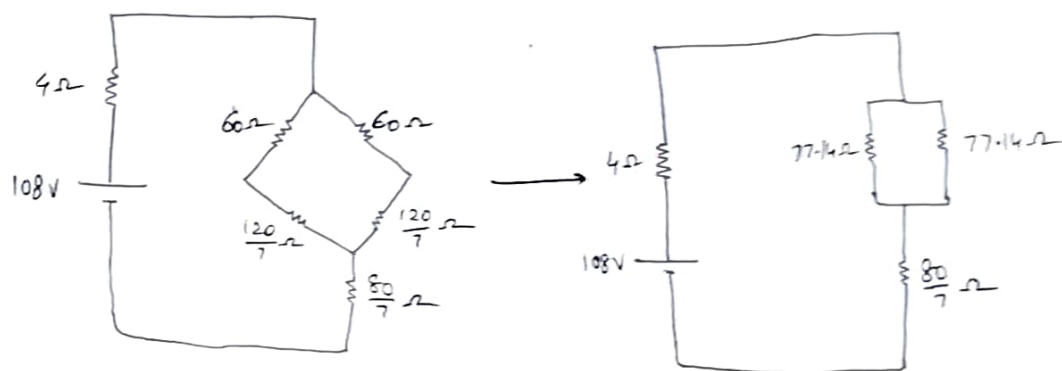


$$I = \frac{108}{54} = 2 \text{ A}$$

$$I = 2 \text{ A}$$

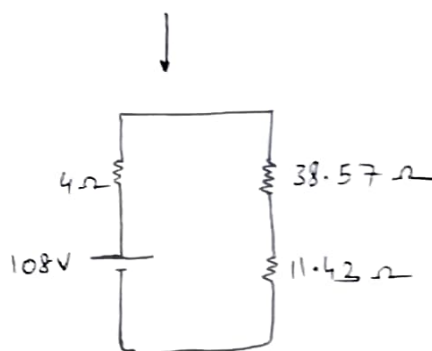





Method ③ (Not in syllabus)

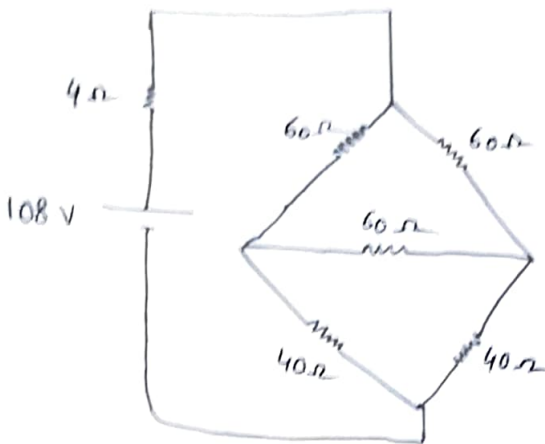

Applying Wheatstone Bridge

$$\frac{P}{Q} = \frac{R}{S}$$

middle one, 60Ω gets removed

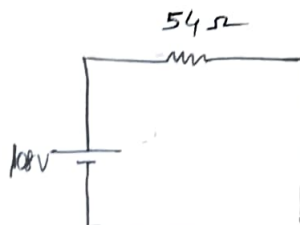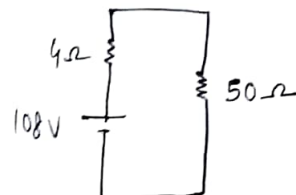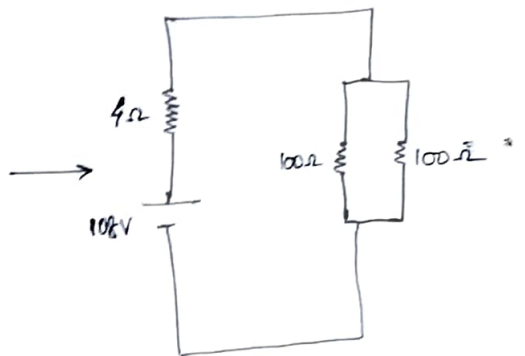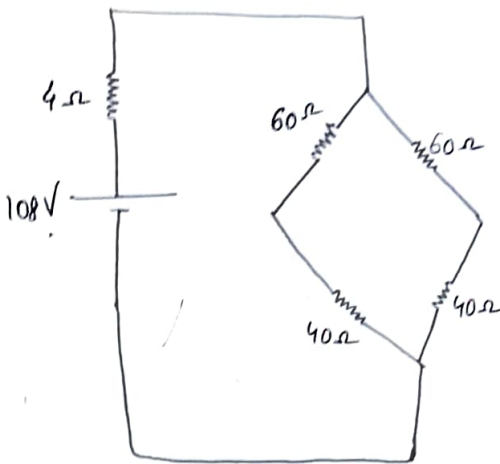

$$i = \frac{V}{R} = \frac{108}{54}$$

$$i = 2A$$